



INDIAN SCHOOL DARSAIT  
DEPARTMENT OF SCIENCE



Subject : PHYSICS Topic : ELECTRICITY REVISION WORKSHEET  
(NUMERICALS)




Resource Person: Mrs. Susan Anil

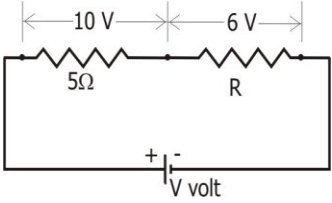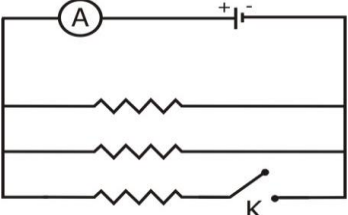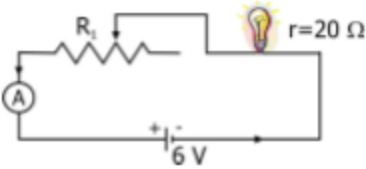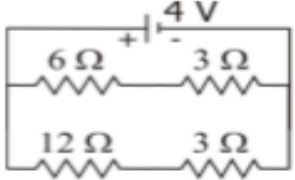

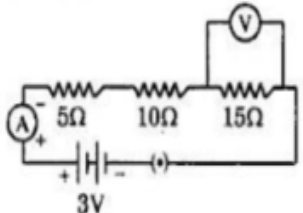
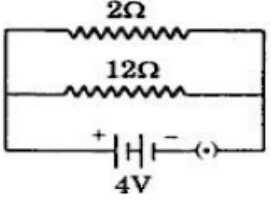
Name of the Student : \_\_\_\_\_ Class & Division : \_\_\_\_\_ Roll Number : \_\_\_\_\_



1.	Two bulbs have ratings 100 W, 220 V and 60 W, 220 V respectively. Which one has a greater resistance? $P = V^2/R$ For the same V, R is inversely proportional to P. Therefore, the bulb 60 W, 220 V has a greater resistance.	1
2.	A Rectangular block of iron has dimensions L X L X b. What is the resistance of the block measured between the two square ends? Given $\rho$ = resistivity. $R = \rho b/L^2$	1
3.	How much energy is given to each coulomb of charge passing through a 9 V battery? $W = VQ = 9 \times 1 = 9 \text{ Joule}$	1
4.	100 J of work is done in moving a charge of 5 C from one terminal of battery to another. What is the potential difference of battery? $V = W/Q = 100/5 = 20 \text{ V}$	1
5.	If $4 \times 10^{-3}$ J of work is done in moving a particles carrying a charge of $16 \times 10^{-6}$ C from infinity to point P .What will be the potential at a point? $V = W/q$ $= (4 \times 10^{-3}) / (16 \times 10^{-6}) = 250 \text{ V}$	1
6.	Calculate the current and resistance of a 100 W, 200V electric bulb. $P = 100W, V = 200V$ $P = VI$ $I = P/V = 100/200 = 0.5A$ $R = V/I = 200/0.5 = 400W$	1
7.	Calculate the power rating of the heater coil when used on 220V supply taking 5 Amps. $V = 220V,$ $P = VI = 220 \times 5 = 1100W = 1.1 \text{ KW}$	1
8.	Calculate the current and resistance of a 100 W, 200V electric bulb. $P = 100W, V = 200V$ $P = VI$ $I = P/V = 100/200 = 0.5A$	1








	$R = V/I = 200/0.5 = 400\Omega$	
9.	Calculate the power rating of the heater coil when used on 220V supply taking 5 Amps. $V = 220V$ , $P = VI = 220 \times 5 = 1100W = 1.1 KW$	1
10.	Calculate the work done in moving a charge of 5 coulombs from a point at a potential of 210 volts to another point at 240 volts. <b>Potential difference = <math>240 - 210 = 30 V</math></b> <b><math>W = V \times Q = 30 \times 5 = 150 J</math></b>	1
11.	Calculate the current supplied by a cell if the amount of charge passing through the cell in 4 seconds is 12 C? $I = Q/t \Rightarrow I = Q/t = 12/4 = 3A$	1
12.	A lamp has a resistance of 96 ohms. How much current flows through the lamp when it is connected to 120 volts? $I = V/R = 120/96 = 1.25 A$ <b>The current through the lamp equals 1.25 A</b>	1
13.	Two resistors X and Y are connected turn by turn: (i) in parallel, and (ii) in series. In which case the resultant resistance will be less than either of the individual resistances? <b>In Parallel combination the resultant resistance will be less than either of the individual resistances.</b>	1
14.	A torch bulb has a resistance of $1 \Omega$ when cold. It draws a current of 0.2 A from a source of 2 V and glows. Calculate (i) the resistance of the bulb when glowing and (ii) explain the reason for the difference in resistance. <b>(i) When the bulb glows: <math>V = IR</math> --- Ohm's law <math>R = V/I = 2/0.2 = 10 \Omega</math></b> <b>(ii) Resistance of the filament of the bulb increases with increase in temperature. Hence when it glows its resistance is greater than when it is cold.</b>	2
15.	A lamp can work on a 50 volt main taking 2 amps. What value of the resistance must be connected in series with it so that it can be operated from 200 volt mains giving the same power? $V = 50V, I = 2A$ $R = V/I = 50 / 2 = 25 \Omega$ <b>Let resistance connected in series with lamp = r</b> $V = 200V, I = 2A$ <b>Total resistance <math>R' = V/I = 200/2 = 100\Omega</math></b> $R' = R + r \Rightarrow 100 = 25 + r \Rightarrow r = 75\Omega$	2
16.	How many electrons pass through a lamp in one minute if the current be 200 mA? $I = 200 mA = 0.22 A$ $I = Q/t \Rightarrow 0.22 = Q/60$ $Q = 0.22 \times 60 = 13.2 C$ <b>No of electron carry 1 C charge = <math>6 \times 10^{18}</math></b>	2





	<b>No of electron carry 13.2 C charge = <math>6 \times 10^{18} \times 13.2 = 79.2 \times 10^{18}</math></b>	
17.	<p>A 2 Volt cell is connected to a <math>1 \Omega</math> resistor. How many electrons come out of the negative terminal of the cell in 2 minutes?</p> <p><b><math>V = IR</math></b>  <b><math>I = V/R = 2/1 = 2 \text{ A}</math></b>  <b><math>I = Q/t \Rightarrow Q = It = 2 \times 2 \times 20 = 80 \text{ C}</math></b>  <b>No of electron carry 1 C charge = <math>6 \times 10^{18}</math></b>  <b>No of electron carry 80 C charge = <math>6 \times 10^{18} \times 80 \text{ C} = 108 \times 10^{18} = 1.08 \times 10^{20}</math></b></p>	2
18.	<p>The potential difference between the terminals of an electric heater is 60 V when it draws a current of 4 A from the source. What current will the heater draw if the potential difference is increased to 120 V?</p> <p><b><math>V = 60 \text{ V}, I = 4 \text{ A}</math></b>  <b><math>R = V/I = 60/4 = 15\Omega</math></b>  <b><math>V' = 120 \text{ V}</math></b>  <b><math>I = V'/R = 120/15 = 8 \text{ A}</math></b>  <b>The current through the heater becomes 8 A</b></p>	2
19.	<p>A <math>4 \Omega</math> resistance wire is doubled on it. Calculate the new resistance of the wire.</p> <p><b><math>R = 4 \Omega, l' = l/2, A' = 2A</math></b>  <b><math>R = \rho(l/A)</math></b>  <b><math>R_1 = R/4 = 4/4 = 1\Omega</math></b></p>	2
20.	<p>A 220V line supplies a total current of 5A to N resistors (each of <math>176\Omega</math>) connected in parallel. What is the value of N?</p> <p><b>The net resistance of N resistors = <math>220/5 = 44\Omega</math></b>  <b><math>R_p = R/N</math></b>  <b><math>N = R/R_p = 176/44 = 4</math></b></p>	2
21.	<p>How many bulbs of <math>8\Omega</math> should be joined in parallel to draw a current of 2A from a battery of 4 V?</p> <p><b><math>N = 4</math></b></p>	2
22.	<p>(a) The manufacturer specifies that a certain lamp will allow 0.8 ampere of current when 120 volts is applied to it. What is the resistance of the lamp?  <b><math>V = IR</math> So, <math>R = V/I = 120/0.8 = 150 \text{ W}</math></b></p> <p>(b) How much voltage is required to cause 1.6 amperes in a device that has 30 ohms of resistance?  <b><math>V = IR = 1.6 \times 30 = 48 \text{ V}</math></b></p> <p style="text-align: center;"><b>(OR)</b></p> <p>(c) How much power is dissipated when 0.2 ampere of current flows through a 100-ohm resistor?  <b><math>P = I^2 R = 0.2 \times 0.2 \times 100 = 4 \text{ W}</math></b></p> <p>(d) How much energy is converted by a device that draws 1.5 amperes from a 12-volt battery for 2 hours?  <b><math>E = VIt = 12 \times 1.5 \times 2 = 36 \text{ Wh}</math></b></p>	2

23.	<p>Two resistances are connected in series as shown in the fig.</p>  <p>(i) What is the current through <math>5\Omega</math> resistor? <b><math>I = V/R = 10/5 = 2A</math></b></p> <p>(ii) What is the current through R? <b><math>I = 2A</math>. In series circuit, current remains the same.</b></p> <p>(iii) What is the value of R? <b><math>R = V/I = 6/2 = 3\Omega</math></b></p> <p>(iv) What is the value of V? <b><math>V = 10 + 6 = 16V</math></b></p>	2
24.	<p>In the diagram, the cell and the ammeter both have negligible resistance. The resistors are identical. With the switch K open, the ammeter reads 0.6 A. What will be the ammeter reading when the switch is closed?</p>  <p>Let <math>I</math> be the current through each resistor. With K open, <b><math>2I = 0.6A</math></b> <b><math>I = 0.6/2 = 0.3A</math></b> With K closed, Current = <b><math>3I = 0.9A</math></b></p>	2
25.	<p>Suppose a 6V battery is connected across a lamp, whose resistance is <math>20\Omega</math>, through a variable resistor as shown in fig. If the current in the circuit is 0.25 A, calculate the value of the resistance from the resistor which must be used.</p>  <p><b>Total Resistance = <math>V/I = 6/0.25 = 24\Omega</math></b> <b><math>R_1 + r = 24</math></b> <b><math>R_1 + 20 = 24</math></b> <b><math>R_1 = 24 - 20 = 4\Omega</math></b></p>	2
26.	<p>Five dry cells each of 1.5 volt have internal resistance of 0.2, 0.3, 0.4, 0.5 and 12 ohms. When connected in series, what current will these five cells furnish through <math>10\Omega</math> resistance?</p>	2

	<p><b>Total <math>V=5 \times 1.5=7.5V</math></b>  <b>Total <math>R=0.2+0.3+0.4+0.5+12=13.4\Omega</math></b>  <b>Current <math>I=V/R=7.5/13.4=75/134 A</math></b></p>	
27.	<p>For the circuit shown in the following diagram, find the value of: (i) Current through <math>6 \Omega</math> resistor. (ii) Potential difference across <math>12 \Omega</math> resistor.</p>  <p>(i) <b>Current across <math>6\Omega</math>, <math>I=4/9A</math></b>  (ii) <b>P.d. across <math>12\Omega</math>, <math>V=4 \times 12/15=16/5V</math></b></p>	2
28.	<p>Calculate the effective resistance between the points A and B in the network shown here.</p>  <p><b><math>1\Omega</math> and <math>2\Omega</math> are in series <math>R_s=3\Omega</math></b>  <b><math>R_p=3 \times 1.5/4.5=1\Omega</math></b></p>	2
29.	<p>What are the likely readings of the ammeter and the voltmeter in the circuit shown here?</p>  <p><b><math>R=5+10+15=30\Omega</math></b>  <b>The ammeter reading = <math>I=V/R=3/30=0.1A</math></b>  <b>The voltmeter reading = <math>V=IR_3=0.1 \times 15=1.5V</math></b></p>	2
30.	<p>Calculate the power used in <math>2\Omega</math> resistor in the circuit shown here.</p>  <p><b>Current through <math>2\Omega</math> <math>I=4/2=2A</math></b>  <b>Power <math>P=V^2/R= 16/2=8W</math></b></p>	2

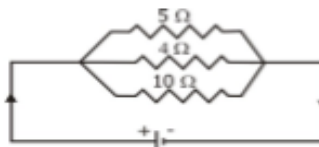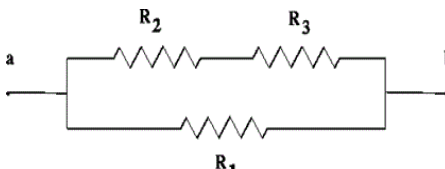31.	<p>When a potential difference of 2 V is applied across the ends of a wire of 5 m length, a current of 1 A is found to flow through it. Calculate: (i) The resistance per unit length of the wire (ii) the resistance of 2 m length of this wire (iii) The resistance across the ends of the wire if it is doubled on itself.</p> <p><b>(i) <math>R = V/I = 2/1 = 2\Omega</math>.</b>  <b>Resistance per unit length: <math>2/5 = 0.4 \Omega/m</math>.</b></p> <p><b>(ii) Resistance of 2 m length of the wire = <math>0.4 \times 2 = 0.8 \text{ ohm}</math></b>  <b>(iii) <math>A_2 = 2 \text{ A}</math> and <math>L_2 = L/2</math></b></p> <p><b>Resistance <math>R' = \rho (l/2)/(2A)</math></b>  <math>= 1/4(\rho(L/A))</math>  <math>= R/4</math>  <b><math>R' = 2/4 = 0.5 \text{ Ohm}</math></b></p>	3
32.	<p>In the circuit diagram given here, the current flowing in <math>5\Omega</math> resistor is 1A. Find the current flowing through the other two resistors.</p>  <p><b><math>V = IR = 1 \times 5 = 5V</math></b>  <b>Current across <math>4\Omega = V/R_2 = 5/4 = 1.25A</math></b>  <b>Current across <math>10\Omega = V/R_3 = 5/10 = 0.5A</math></b></p>	3
33.	<p>How will you connect three resistors of <math>2\Omega</math>, <math>3\Omega</math> and <math>5\Omega</math> respectively so as to obtain a resultant resistance of <math>2.5 \Omega</math>? Draw the diagram to show the arrangement.</p> <p><b><math>2\Omega</math>, <math>3\Omega</math> are in series and parallel to <math>5\Omega</math></b></p>  <p>Two resistances when connected in parallel give resultant value of <math>2\Omega</math>. When they are connected in series, the value becomes <math>9 \Omega</math>. Calculate the value of each resistance.</p> <p><b>For Series,</b>  <math>R_1 + R_2 = 9 \dots \dots \dots (1)</math></p> <p><b>For Parallel,</b></p> $\frac{R_1 R_2}{R_1 + R_2} = 2$ $\frac{R_1 R_2}{9} = 2$ <p><b><math>R_1 R_2 = 18</math></b></p> $(R_1 - R_2)^2 = (R_1 + R_2)^2 - 4R_1 R_2$ $(R_1 - R_2)^2 = 81 - 72$ $(R_1 - R_2)^2 = 9$	3

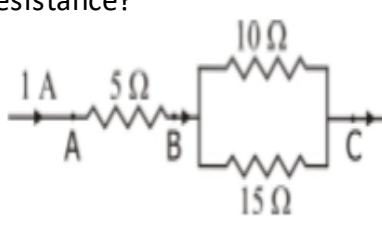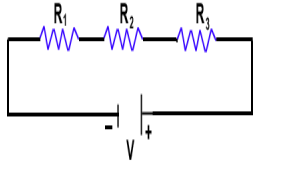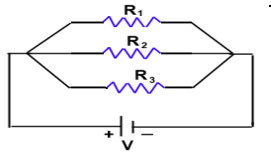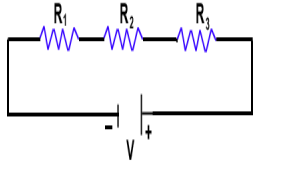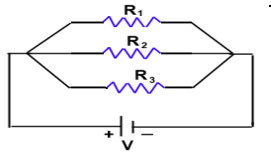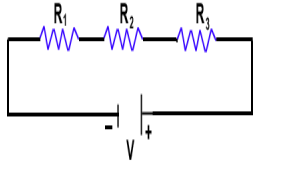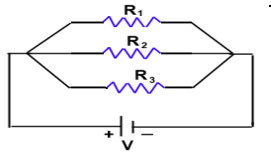	<p><math>R_1 - R_2 = 3</math>------(2)</p> <p><b>Solving (1) &amp; (2)</b>  <math>2R_1 = 6</math>  <math>R_1 = 3\Omega, R_2 = 3\Omega</math></p>					
34.	<p>Three resistors are connected as shown in the diagram. Through the resistor 5 ohm, a current of 1 ampere is flowing.</p> <p>(i) What is the current through other two resistors?  (ii) What is the p.d. across AB and across AC?  (iii) What is the total resistance?</p>  <p>(i) Resistance across parallel combination <math>R_p = 6\Omega</math>  <math>V_{BC} = IR_p = 1 \times 6 = 6V</math>  As p.d. across parallel combination remains same,  <math>10I_1 = 6</math>  <math>I_1 = 0.6A</math>  <math>15I_2 = 6</math>  <math>I_2 = 0.4A</math></p> <p>(ii) <math>V_{AB} = 1 \times 5 = 5V</math> ; <math>V_{AC} = 11V</math></p> <p>(iii) <math>10\Omega</math> and <math>15\Omega</math> are parallel</p> $R_p = \frac{R_1 R_2}{R_1 + R_2} = \frac{10 \times 15}{10 + 15} = \frac{150}{25} = 6\Omega$ <p>Total resistance = <math>5 + 6 = 11\Omega</math></p>	3				
35.	<p>You are given three resistances of 1, 2 and 3 ohms. Show by diagrams, how with the help of these resistances you can get: (i) 6 <math>\Omega</math>, (ii) 6/11 <math>\Omega</math>, (iii) 1.5 <math>\Omega</math>, (iv) 4/3 <math>\Omega</math>, (v) 5/6 <math>\Omega</math>, (vi) 11/5 <math>\Omega</math></p> <table border="1" data-bbox="223 1523 1324 1926"> <tr> <td data-bbox="223 1523 989 1747">all in series</td> <td data-bbox="989 1523 1324 1747">  </td> </tr> <tr> <td data-bbox="223 1747 989 1926">all in parallel</td> <td data-bbox="989 1747 1324 1926">  </td> </tr> </table>	all in series		all in parallel		3
all in series						
all in parallel						
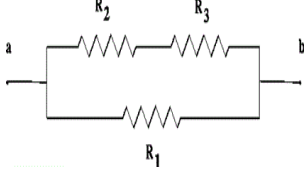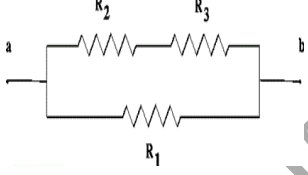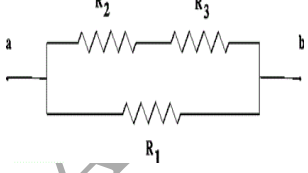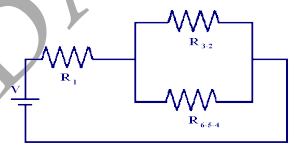
<p><b>1Ω &amp; 2Ω in series and the combination is parallel to 3Ω</b></p>			
<p><b>1Ω &amp; 3Ω in series and the combination is parallel to 2Ω</b></p>			
<p><b>2Ω &amp; 3Ω in series and the combination parallel to 1Ω</b></p>			
<p><b>parallel combination of 2 Ω and 3 Ω in series with 1 Ω</b></p>			

INDIAN SCHOOL DRY